



max planck institut
informatik

Designing Low-Noise Analog Electronics for Time and Frequency Metrology

Attila Kinali

2020-07-19

Measurement

What does measuring mean?

The process of taking an *analog* signal, *processing* it and recording *numerical* (digital) data is called *measuring*.

Measurements in the Past vs Today

The past:

- Digital electronics slow and expensive
- ADCs were slow, noisy and low resolution

→

- Lots of analog processing
- Late digitalization


Today:

- Digital electronics cheaper than analog
- ADCs fast, low noise and high resolution


→

- Little analog processing
- Early digitalization


Limiting Amplifier

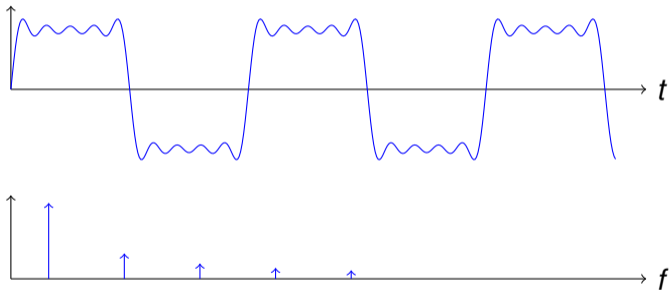

Limiting Amplifier

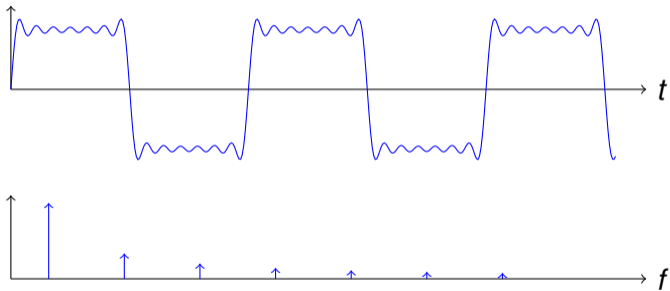


Noise Folding Due to Harmonics

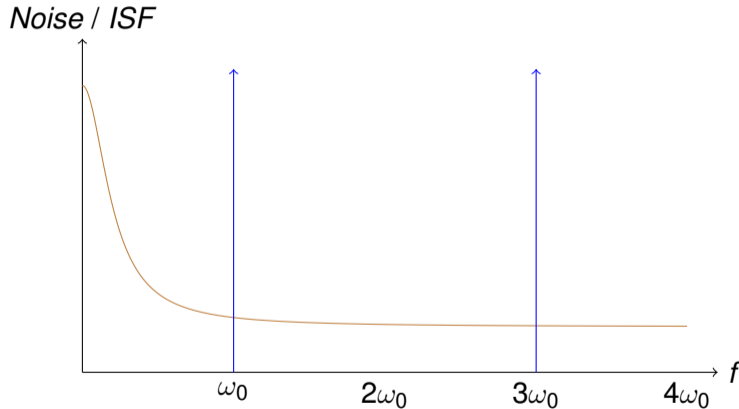


[Hajimir & Lee 1998]
[Kinali 2018 & 2019]

Noise Folding Due to Harmonics

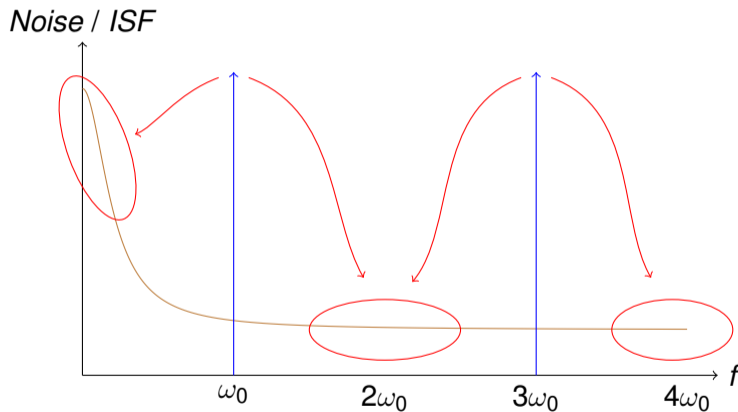


[Hajimir & Lee 1998]
[Kinali 2018 & 2019]

Noise Folding Due to Harmonics

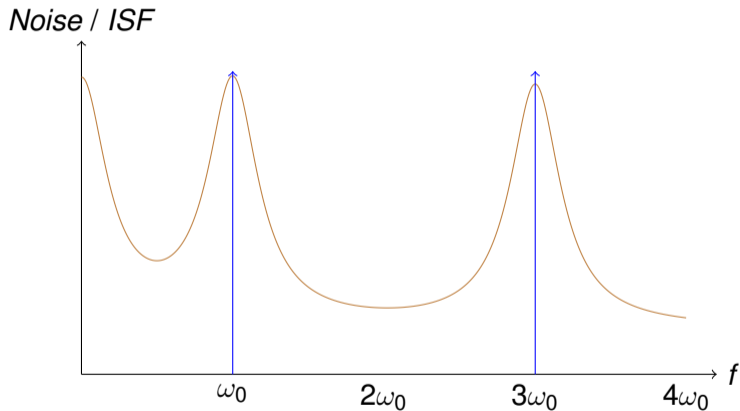


[Hajimir & Lee 1998]
[Kinali 2018 & 2019]


Multistage?

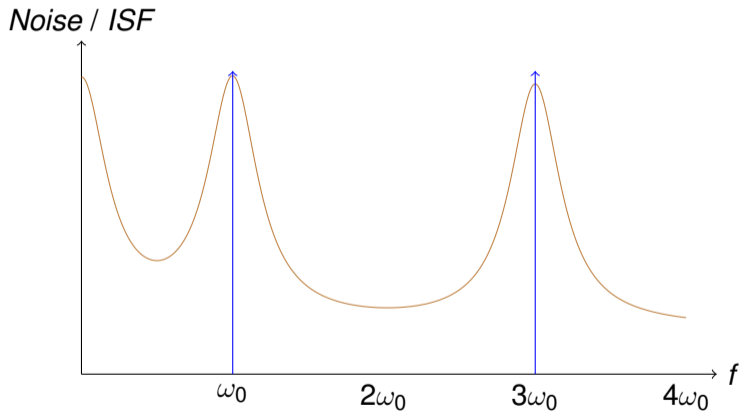


Multistage?

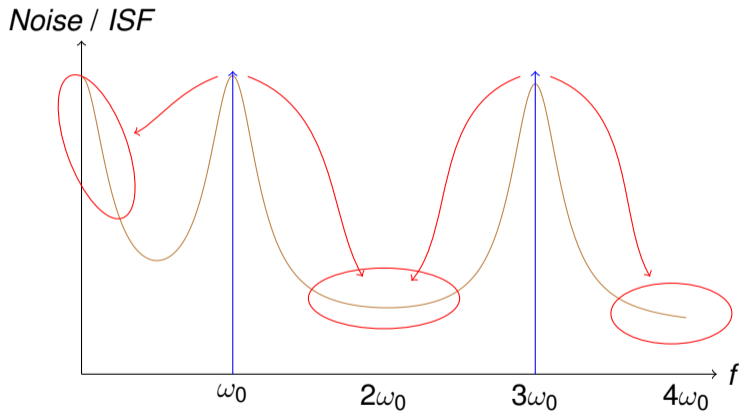


Multistage with duty cycle $\neq 50\%$

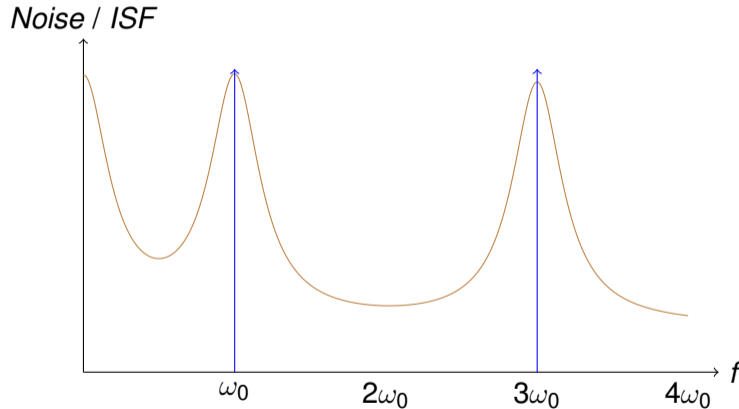

Multistage with duty cycle $\neq 50\%$

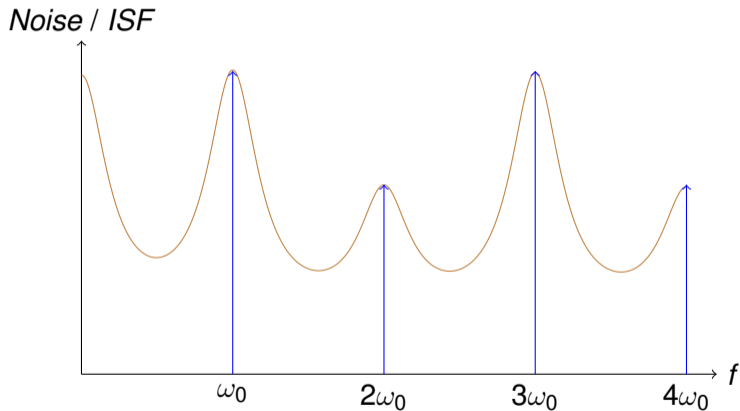

Multistage with duty cycle $\neq 50\%$

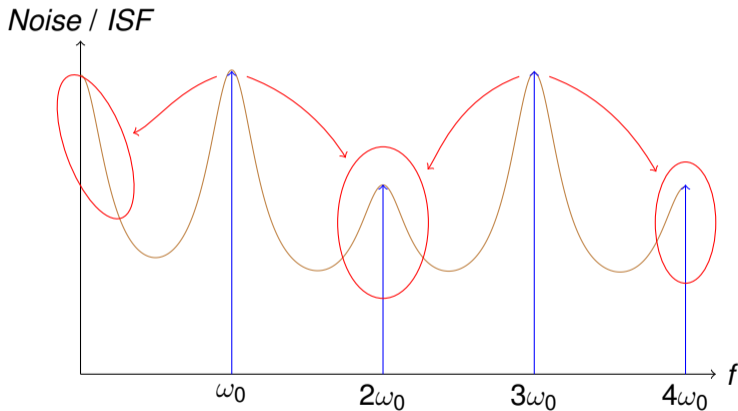


How to Design an Amplifier


Signal frequency and bandwidth:

- Low frequency:
 - Opamps offer low noise and ease of use
 - Use discrete transistor pre-amp for lower noise
 - Use differential signaling for high power supply rejection
 - Add differential-drift cancelation circuit for second harmonic suppression
- High frequency:
 - Opamps are noisy, but might be good enough
 - MMIC amplifiers available with low noise figure
 - Use discrete transistor amplifiers if possible
 - Use push-pull architecture for second harmonic suppression


Differential Low Frequency Amplifier

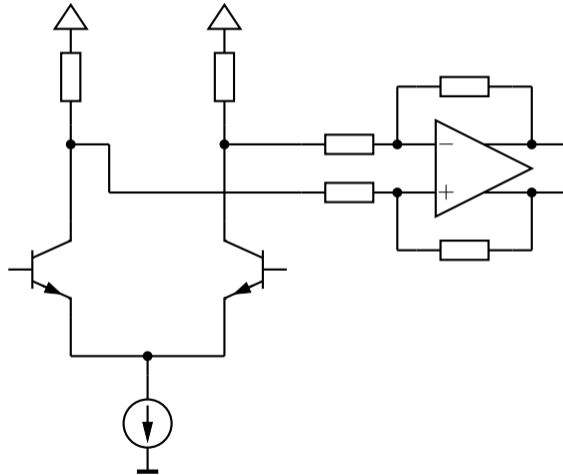


High Frequency Amplifier

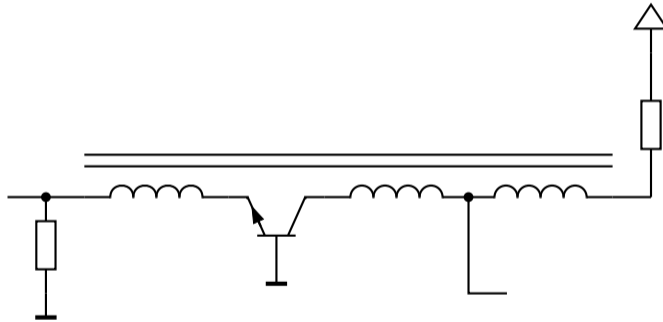



High Frequency Amplifier

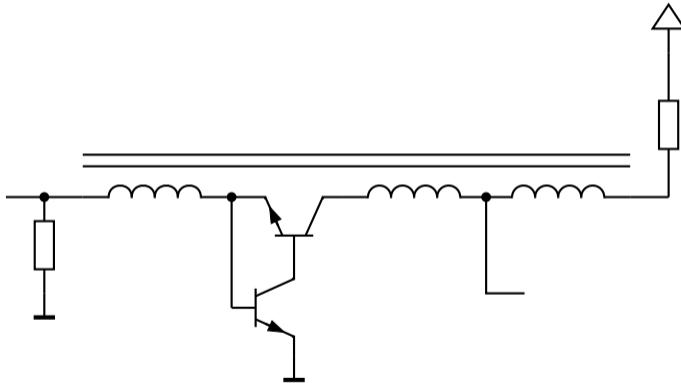


Push-Pull High Frequency Amplifier

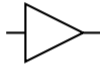

Push-Pull High Frequency Amplifier

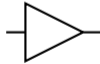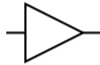




Push-Pull High Frequency Amplifier

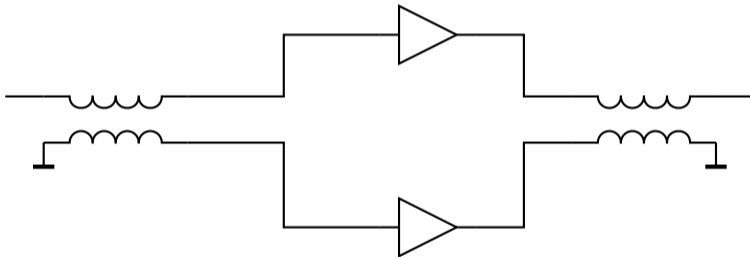

Things We Have Not Talked About

- Power supplies (linear vs switched)
- Digital signal processing and its noise and non-linearities
- How to find the right architecture
- Component selection
- How to estimate the noise performance of the circuit

Further Reading

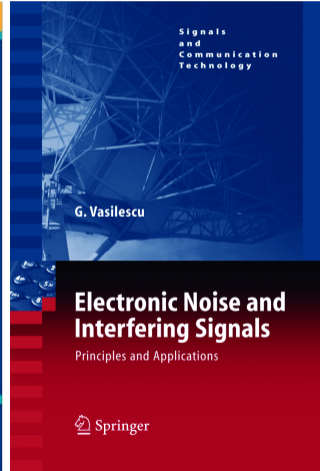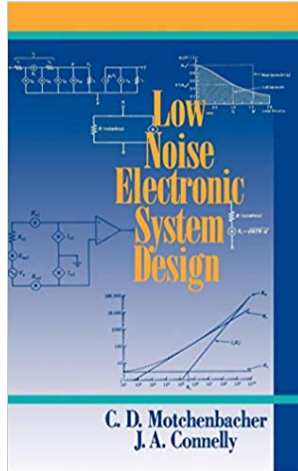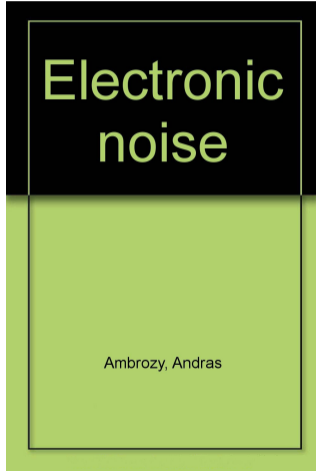

Further Reading

